

III B. TECH II SEMESTER REGULAR EXAMINATIONS APRIL - 2023
DIGITAL ELECTRONICS
(ELECTRICAL AND ELECTRONICS ENGINEERING)

Time: 3 hours

Max. Marks: 70

Note: Answer **ONE** question from each unit (**5 × 14 = 70 Marks**)

~~~~~

UNIT-I

1. a) i) Convert  $(F57)_{16}$  into decimal. [7M]  
 ii) Convert  $(6348)_{10}$  into Octal.  
 b) Obtain the 9's and 10's complement of  $(389.61)_{10}$ . [7M]

(OR)

2. a) i) List the truth table of  $F = (xy + xy' + y'z)'$  [7M]  
 ii) Draw logic diagrams to implement the Boolean expression  $Y = A + B + B'(A + C')$   
 b) Implement the given function using NOR gates only. [7M]  
 $F(X, Y, Z) = \sum m(0, 3, 6)$ .

UNIT-II

3. a) Obtain the simplified expression in product of sums. [7M]  
 $F(A, B, C, D) = \pi(0, 2, 5, 6, 9, 12, 13)$   
 b) Obtain the simplified expression in sum of products for the following [7M]  
 Boolean function.  
 $BDE + B' C' D + CDE + A' B' CE + A' B' C + B' C' D' E'$

(OR)

4. a) Using K-map method, Reduce the following Boolean function. [7M]  
 $F = \sum m(0, 2, 3, 6, 7) + d(8, 10, 11, 15)$  and obtain minimal SOP  
 b) Explain a four-bit binary adder circuit with relevant [7M]  
 diagram.

UNIT-III

5. a) Design the logic circuit for full subtractor using truth table. [7M]  
 b) Implement a 2-bit magnitude comparator [7M]

(OR)

- 6. a) Design 16 x 4 encoders using two 8 x 3 encoders. [7M]
- b) Implement Boolean function  $F(A,B,C,D)=\Sigma m(0,1,3,4,8,9,15)$  using 8:1 multiplexer. [7M]

UNIT-IV

- 7. a) Design MOD-10 asynchronous counter using JK flipflop. [7M]
- b) Explain in detail the operation of a 4-bit binary ring counter. [7M]

(OR)

- 8. a) Design a D flip flop using JK flip flop and explain with its truth table [7M]
- b) What is shift register? Explain the working of 4-bit bidirectional shift register. [7M]

UNIT-V

- 9. a) Explain state diagram, state table and state assignment with example. [7M]
- b) Write difference between Mealy and Moore machines in detail. [7M]

(OR)

- 10. a) Design an FSM for serial sequence detector with the pattern "0110" with non-overlapping. use Mealy Machine. [7M]
- b) Write design procedure of a finite state machine. [7M]

\* \* \* \* \*